Student's Name:

Introduction to circuit analysis


Homework 9 - Equivalent capacitance and inductance, and RC Transient circuit

Instructions:


- O YOU HAVE TO SHOW ALL WORK IN ORDER TO RECEIVE FULL CREDIT
- o All answer must be in engineering notation rounded off to the hundredth

Question 1) For the following circuit, find the equivalent capacitance


a)

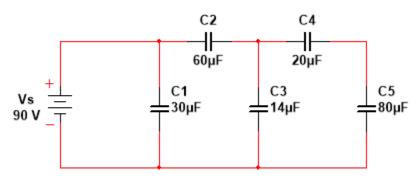

b)

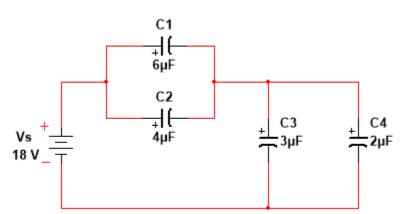


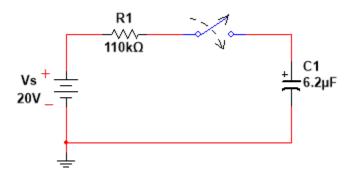
Question 2) For the following RC transient circuit, find the voltage and current through the resistor and the voltage drop at the capacitor, according the given time in the table.




RC Transient Circuit			
Time (ms)	$v_C = V_S \left(1 - \mathbf{e}^{-\frac{t}{RC}} \right)$	$v_R = V_S \left(\mathbf{e}^{-\frac{t}{RC}} \right)$	$i_C = \frac{V_S}{R} \left(e^{-\frac{t}{RC}} \right)$
0			
150			
400			
600			
800			
1000			
2200			
3200			
4200			

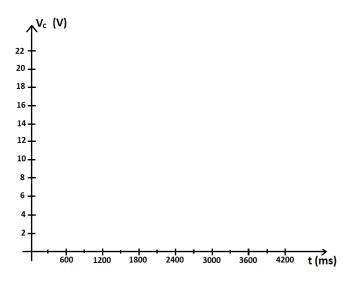Use the table above, sketch V_{C} , I_{C} , and V_{R}



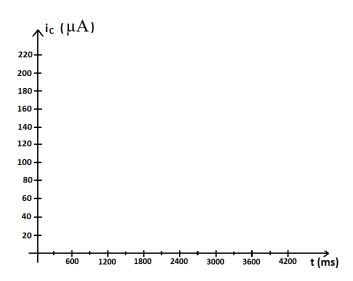

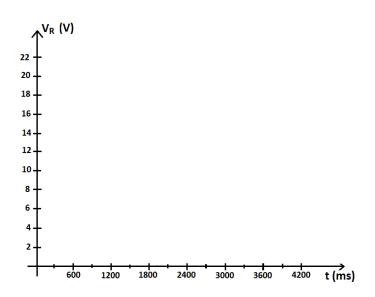

------ Homework Ends Here ------